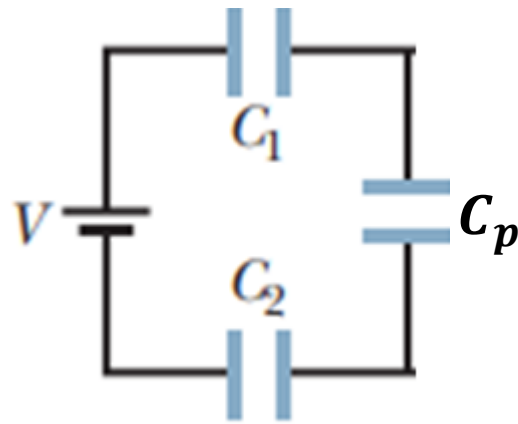



Lecture 12

Chapter 25
Math Problems

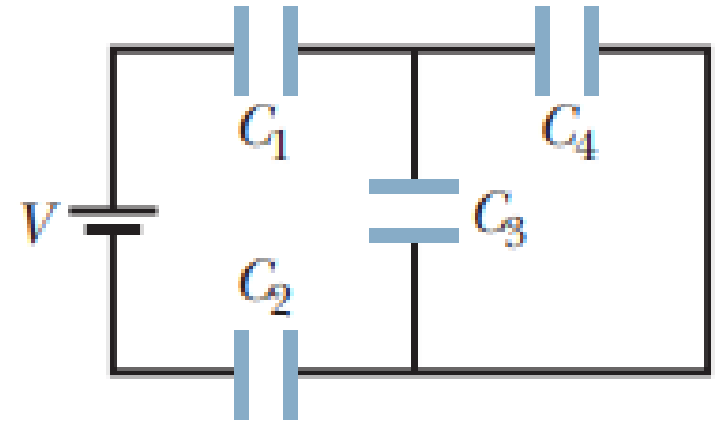Q1. In Fig. , $V = 9.0\text{ V}$, $C_1, C_2 = 30\text{ }\mu\text{F}$, and $C_3, C_4 = 15\text{ }\mu\text{F}$.
What is the charge on capacitor 4?




$$\begin{aligned} C_p &= C_3 + C_4 \\ &= 15 + 15 \\ &= 30\text{ }\mu\text{F} \end{aligned}$$



$$\begin{aligned} \frac{1}{C_s} &= \frac{1}{C_1} + \frac{1}{C_p} + \frac{1}{C_2} \\ &= \frac{1}{30} + \frac{1}{30} + \frac{1}{30} \end{aligned}$$

$$\begin{aligned} &= \frac{3}{30} \\ &= \frac{1}{10} \end{aligned}$$

$$C_s = 10\text{ }\mu\text{F}$$

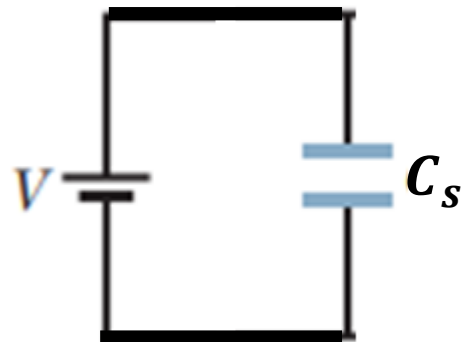


$$\begin{aligned} q_s &= C_s V = 10 \times 10^{-6} \times 9 = 90 \times 10^{-6}\text{ C} \\ \text{Therefore, } q_p &= 90 \times 10^{-6}\text{ C} \end{aligned}$$


$$\begin{aligned} q_p &= C_p V_p \\ V_p &= \frac{q_p}{C_p} = \frac{90 \times 10^{-6}}{30 \times 10^{-6}} = 3\text{ V} \end{aligned}$$

$$\begin{aligned} \text{Therefore, potential difference on } C_3 \text{ and } C_4 &\text{ are } 3\text{ V} \\ \text{So, } q_4 &= C_4 V_p = 15 \times 10^{-6} \times 3 = 45 \times 10^{-6}\text{ C} = 45\text{ }\mu\text{C} \end{aligned}$$

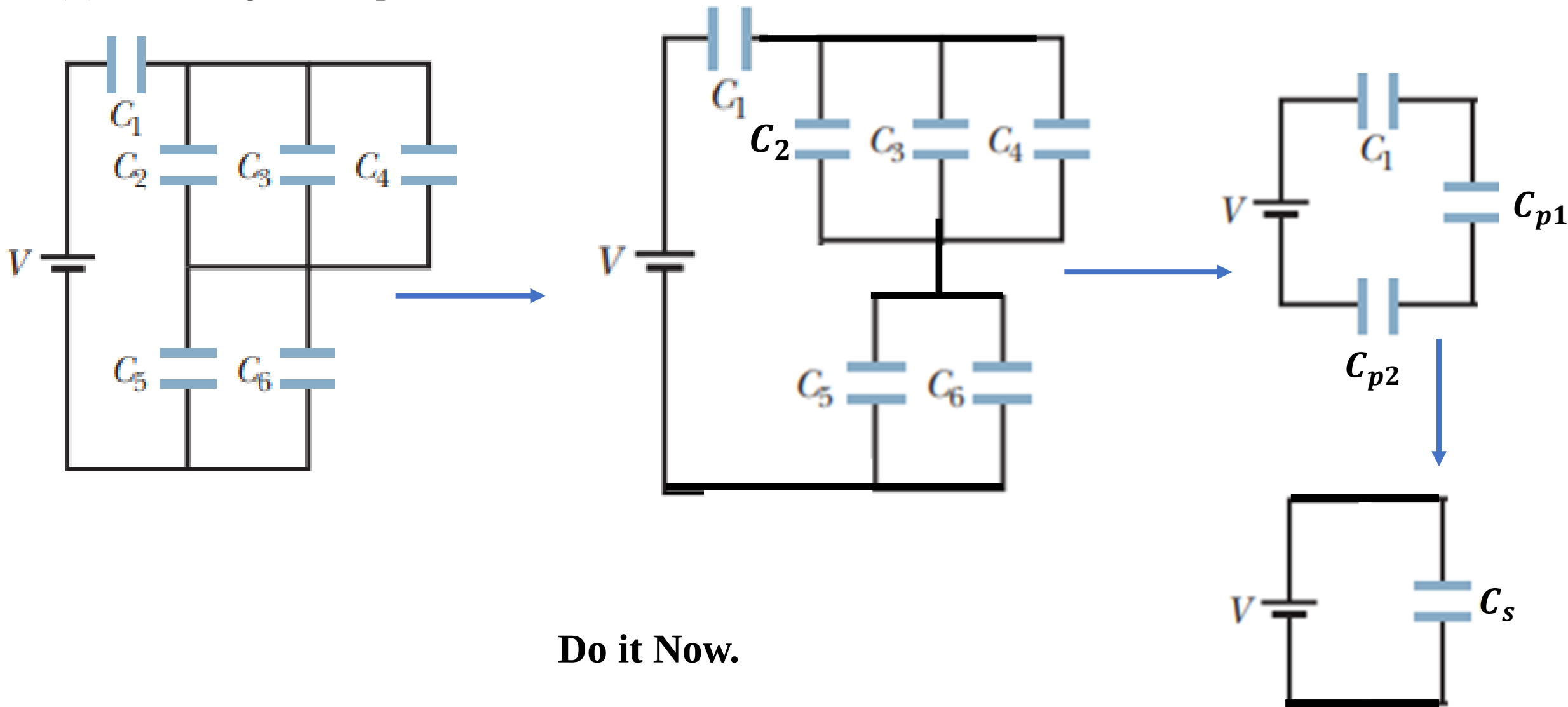Q2. In Fig. , $V = 12\text{ V}$, $C_1, C_5, C_6 = 6.0\text{ }\mu\text{F}$, and $C_2, C_3, C_4 = 4.0\text{ }\mu\text{F}$. What are (a) the net charge stored on the capacitors and (b) the charge on capacitor 4?



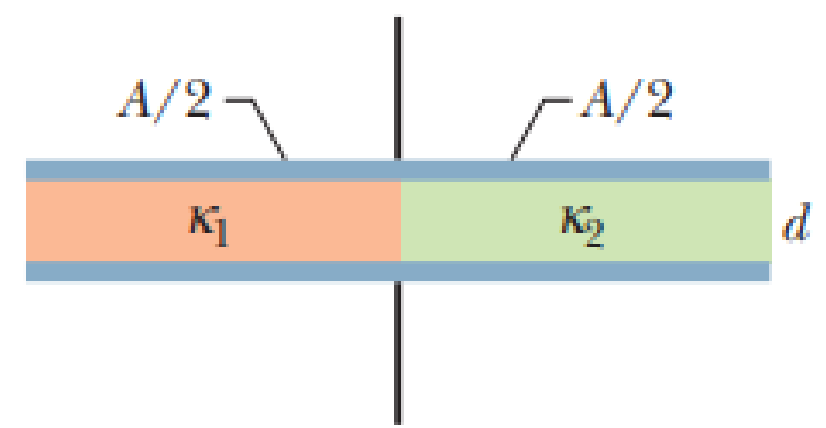Q3. Figure shows a parallel plate capacitor with a plate area $A = 5.56 \text{ cm}^2$ and separation $d = 5.56 \text{ mm}$. The left half of the gap is filled with material of dielectric constant $k_1 = 7.00$; the right half is filled with material of dielectric constant $k_2 = 12.0$. What is the capacitance?




Let, the capacitance of capacitors of left side and right are C_1 and C_2

$$C_1 = \frac{\epsilon_0 k_1 \frac{A}{2}}{d} = \frac{\epsilon_0 k_1 A}{2d} = \frac{8.854 \times 10^{-12} \times 7 \times 5.56 \times 10^{-4}}{2 \times 5.56 \times 10^{-3}} = 3.1 \times 10^{-12} F$$

$$C_2 = \frac{\epsilon_0 k_2 \frac{A}{2}}{d} = \frac{\epsilon_0 k_2 A}{2d} = \frac{8.854 \times 10^{-12} \times 12 \times 5.56 \times 10^{-4}}{2 \times 5.56 \times 10^{-3}} = 5.31 \times 10^{-12} F$$

$$C_p = C_1 + C_2 = 3.1 \times 10^{-12} + 5.31 \times 10^{-12} = 8.41 \times 10^{-12} F$$

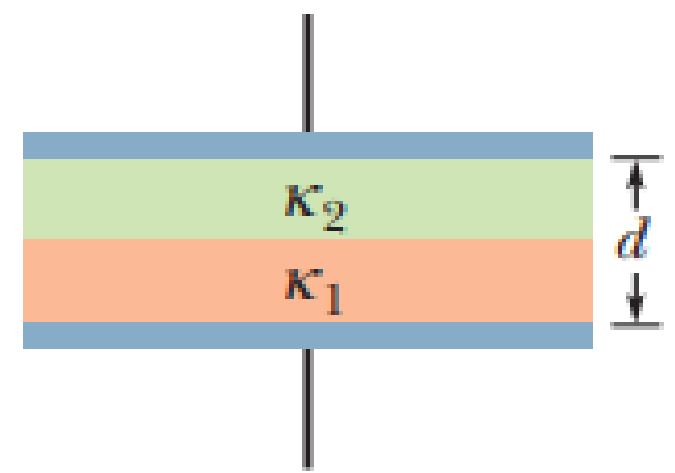Q4. Figure shows a parallel-plate capacitor with a plate area $A = 7.89 \text{ cm}^2$ and plate separation $d = 4.62 \text{ mm}$. The top half of the gap is filled with material of dielectric constant $k_1 = 11.0$; the bottom half is filled with material of dielectric constant $k_2 = 12.0$. What is the capacitance?



Let, the capacitance of capacitors of bottom and top zone are C_1 and C_2

$$C_1 = \frac{\epsilon_0 k_1 A}{\frac{d}{2}} = \frac{2\epsilon_0 k_1 A}{d} = \frac{2 \times 8.854 \times 10^{-12} \times 11 \times 7.89 \times 10^{-4}}{4.62 \times 10^{-3}}$$

$$= 3.32 \times 10^{-11} \text{ F}$$

$$C_2 = \frac{\epsilon_0 k_2 A}{\frac{d}{2}} = \frac{2\epsilon_0 k_2 A}{d} = \frac{2 \times 8.854 \times 10^{-12} \times 12 \times 7.89 \times 10^{-4}}{4.62 \times 10^{-3}}$$

$$= 3.63 \times 10^{-11} \text{ F}$$


$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_s = \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{3.32 \times 10^{-11} \times 3.63 \times 10^{-11}}{3.32 \times 10^{-11} + 3.63 \times 10^{-11}}$$


$$C_s = 1.73 \times 10^{-11} \text{ F}$$

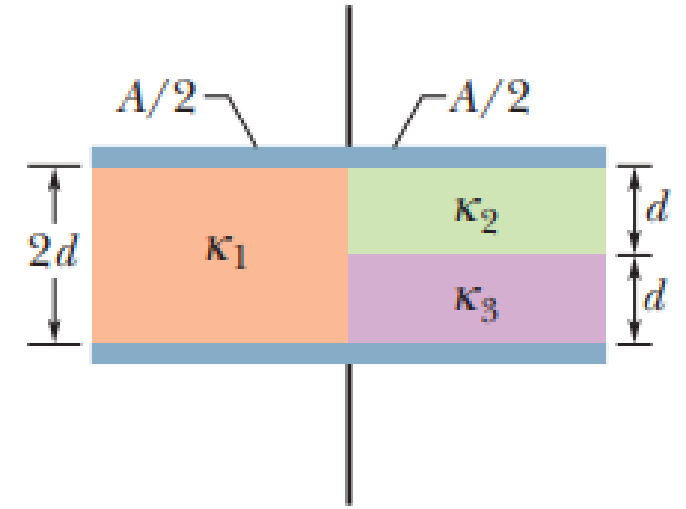Q5. Figure shows a parallel-plate capacitor of plate area $A = 10.5 \text{ cm}^2$ and plate separation $2d = 7.12 \text{ mm}$. The left half of the gap is filled with material of dielectric constant $k_1 = 21.0$; the top of the right half is filled with material of dielectric constant $k_2 = 42.0$; the bottom of the right half is filled with material of dielectric constant $k_3 = 58.0$. What is the capacitance?



Do it Now

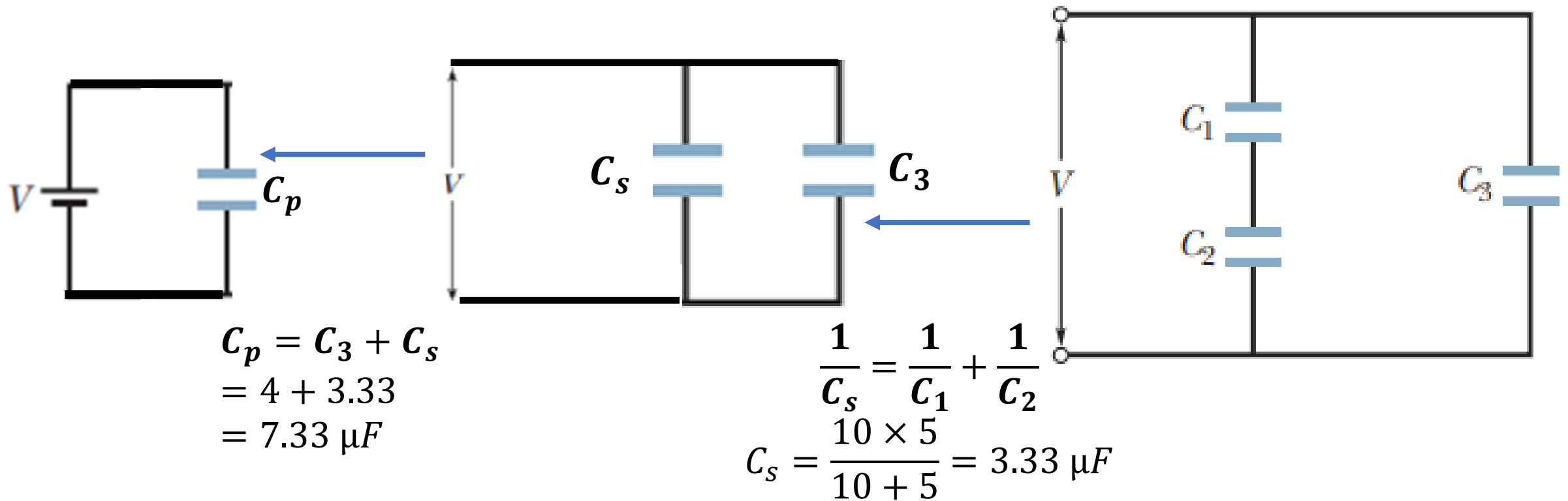Q6. In Fig, a potential difference $V = 100\text{ V}$ is applied across a capacitor arrangement with capacitances $C_1 = 10\text{ }\mu\text{F}$, $C_2 = 5.0\text{ }\mu\text{F}$, and $C_3 = 4.0\text{ }\mu\text{F}$. What are (a) charge q_3 , (b) potential difference V_3 , and (c) stored energy U_3 for capacitor 3, (d) q_1 , (e) V_1 , and (f) U_1 for capacitor 1, and (g) q_2 , (h) V_2 , and (i) U_2 for capacitor 2?



Do it Now

Thank You